# DVB-T Receiver With a Fully Digital I/Q Separator\*

Chua-Chin Wang<sup>1,†</sup>, Senior Member, IEEE, Ming-Kai Chang<sup>1</sup>, and Tsai-Wen Cheng<sup>1</sup>

Abstract -- This paper describes the design of a digital I/Q separator which is applied to DVB-T receivers. The proposed I/Q separator not only avoids problems caused by analog I/Q separators, e.g., gain error, phase error, DC offset, etc., it also resolves the difficulties of prior digital I/Q separators, e.g., large area, large gate count, and high power consumption by insertion of decimation filters. A prototypical system as well as a chip has been designed using 0.18-μm single-poly six-metal CMOS process with core area of 1.59 mm². The total power consumption is merely 433 μW at a 20.0 MHz system clock.

Key word: demodulation, I/Q separator, decimation filter, DVB-T, wireless network

#### I. INTRODUCTION

I/Q separator plays a very important role in most of the demodulators for wireless communication systems. The traditional analog quadrature demodulator with analog-to-digital converters (ADCs) is illustrated in Fig. 1. The intermediate frequency (IF) input signal, s(t), is mixed with the local oscillator (LO) and a 90 degree delayed signal of the same frequency. Two orthogonal channels known as the inphase (I) channel and the quadrature-phase (Q) channel are generated. Several problems in which a traditional analog I/Q separator have been recognized, e.g., gain error, phase error [4], and DC offset [1]. By contrast, fully digital I/Q separators like Hilbert transform [2], band-pass signal [2] and decimation filter [2], can dodge these problems but pay the expense of large area, large gate count, and high power consumption.

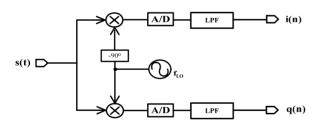


Fig. 1. Conventional analog I/Q separator

## II. FULLY DIGITAL I/Q SEPARATOR DESIGN

Fig. 2 shows a traditional digital I/Q separator. The basic component has an ADC, an LO, two multipliers, and two low-pass filters (LPF). We will transform such an architecture into

a fully digital I/Q separator through detailed analysis both in time domain and frequency domain.

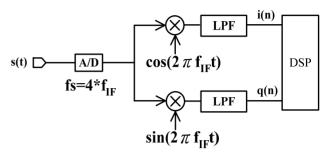


Fig. 2. Traditional digital I/Q separator

## A. Local Oscillator

The local oscillator (LO) frequency is set to be 1/4 of the ADC conversion frequency. Fig. 3 shows that the mixing in I channel between the output of the ADC and the LO is simplified to be a multiplication with a sequence of +1, 0, -1, 0... By contrast, the mixing in O channel becomes a multiplication with a sequence of 0, -1, 0, +1.... The LO signal generation is now degenerated to be a trivial digital operation, while the multipliers implementing the mixers in Fig. 2 are reduced to a circuit that simply passes, nullifies or reverses the sign of the data. For instance, at t = 0, the input signal is multiplied by +1 in the I channel and 0 in the Q channel. At t=T/4, the input signal is multiplied by +1 in the Q channel and 0 in the I channel, meaning that this sample is fed directly to the Q channel. At t = T/2, the signal is multiplied by -1 and fed to the I channel. Last at t = 3T/4, the signal is inverted and fed to the O channel. This sequence is constantly repeated to produce the continuous I and Q streams.

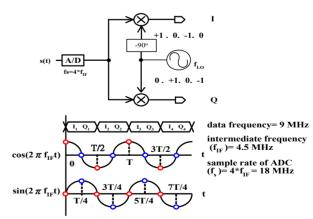


Fig. 3. LO simplification

In short, the sequence after the proper inversion and

<sup>\*</sup> This research was partially supported by the National Heath Research Institutes under grant NHRI-EX94-9319EI and National Science Council under grant NSC 94-2213-E-110-022 and NSC 94-2213-E-110-024.

<sup>&</sup>lt;sup>1</sup> C.-C. Wang. M.-K. Chang, and T.-W. Zheng are with Department of Electrical Engineering, National Sun Yat-Sen University, 80424, Taiwan. (e-mail: <a href="mailto:ccwang@ee.nsysu.edu.tw">ccwang@ee.nsysu.edu.tw</a>).

shuffling becomes the following stream.

$$I_1, Q_1, -I_2, -Q_2, I_3, Q_3, -I_4, -Q_4...$$
 (1)

#### B. Decimation Filter

In prior digital I/Q separators as shown in Fig. 2, a decimation filter which serves as the LPF is required. After system simulations, it is found a 41-tap LPF is needed for DVB-T receivers to subside the ripples. Assume  $h_0, h_1..., h_{40}$  are the coefficient of the filter. Top of Fig. 4 shows that only  $h_0, h_2, h_4..., h_{2n}$ , for all n = 1..., 20, are needed in the computation of I channel. By contrast, the bottom of Fig. 4 shows the same for Q channel. In short, the LPF needs only the even-numbered terms (coefficients).

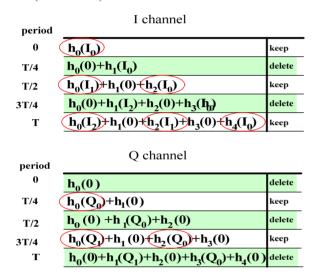


Fig. 4. The operation of decimation filter

Fig. 5 shows the impulse response of the decimation filter with 41-tap, where only h<sub>20</sub> is 0.5, the rest of coefficients are 0. Therefore, the coefficients of decimation filter can be simplified to a divided-by-2 operation to carry out the coefficient, 0.5. In summary, the correct stream of I and Q can be generated after the outputs of the mixers are multiplied with 0.5. Thus, the complicated digital I/Q separator in Fig. 2 can be simplified to be the I/Q separator in Fig. 6. The multiplier, LPF, a phase shifter, and an LO are no longer needed to reduce area as well as power.

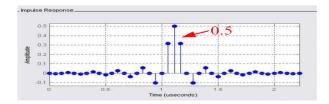


Fig. 5. Impulse response of decimation with 41-tap

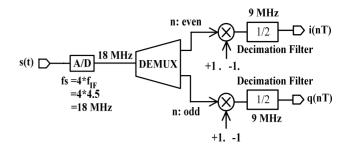


Fig. 6. Structure of the proposed

## III. IMPLEMENTATION AND SIMULATION RESULT

The proposed design is carried out by FPGA and TSMC (Taiwan Semiconductor Manufacturing Company)  $0.18~\mu m$  single-poly six-metal CMOS technology. The specifications of the proposed design is summarized in Table 1. Table 2 shows the comparison between a prior work and the our design.

TABLE I
SPECIFICATIONS OF THE PROPOSED DIGITAL I/Q SEPARATOR

Technology
Power supply
1.8 V
Clock frequency
Core size
Power consumption @ 20MHz
433 µW

TABLE II

COMPARISON BETWEEN THE PRIOR SCHEME AND THE PROPOSED

Design Die size Power Power consumption Technology

Design	Die size	Power supply	Power consumption	Technology
Ours	1.24×	1.8 V	433 μW	TSMC 0.18
	1.28mm <sup>2</sup>			um 1p6m
[3]	4.7×	5V	1.5 mW	1.2 um
	7.7mm <sup>2</sup>	3 V	1.3 IIIW	CMOS

## ACKNOWLEDGMENT

The authors would like to express their deepest gratefulness to CIC of NSC for their thoughtful chip fabrication service. The authors also like to thank "Aim for Top University Plan" project of NSYSU and MOE, Taiwan, for partially supporting this investigation.

### REFERENCE

- D. W. Rice., and K. H. Wu, "Quadrature sample with high dynamic range," *IEEE Trans. On Aerospace and Electronic Systems*. vol. AES-18, no. 4, pp. 736-739, Nov. 1982.
- [2] T. E. Thiel, and G. J. Saulnier, "Simplified complex digital sampling demodulato," *Electronics Letters*, vol. 26 no. 7, pp. 419-421, Mar. 1990.
- [3] B. C. Wong and H. Samueli," A 200-MHz all digital QAM modulator and demodulator in 1.2-μm CMOS for digital radio applications," *IEEE J. of Solid-State Circuits*, vol. 26, no. 12, pp. 1970-1980, Dec. 1991.
- [4] A. Schuchert, R. Makowitz, and M. Buchholz, "Front end architectures for multistandard digital TV receivers," *IEEE Trans. On Consumer Electronics*, vol. 46, no. 3, pp. 422-427, Aug. 2000.